

# Functional Blocks: Addition

---

- **Binary addition used frequently**
- **Addition Development:**
  - *Half-Adder (HA)*, a 2-input bit-wise addition functional block,
  - *Full-Adder (FA)*, a 3-input bit-wise addition functional block,
  - *Ripple Carry Adder*, an iterative array to perform binary addition, and
  - *Carry-Look-Ahead Adder (CLA)*, a hierarchical structure to improve performance.

# Functional Block: Half-Adder

- A 2-input, 1-bit width binary adder that performs the following computations:

<b>X</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>+ Y</b>	<b>+ 0</b>	<b>+ 1</b>	<b>+ 0</b>	<b>+ 1</b>
<b>C S</b>	<b>0 0</b>	<b>0 1</b>	<b>0 1</b>	<b>1 0</b>

- A half adder adds two bits to produce a two-bit sum
- The sum is expressed as a sum bit , S and a carry bit, C
- The half adder can be specified as a truth table for S and C  $\Rightarrow$

<b>X</b>	<b>Y</b>	<b>C</b>	<b>S</b>
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>

# Logic Simplification: Half-Adder

- The K-Map for S, C is:
- This is a pretty trivial map!  
By inspection:

S		Y	
	0	1 <sub>1</sub>	
X	1 <sub>2</sub>		3

C		Y	
	0	1	
X	2	1 <sub>3</sub>	

$$S = X \cdot \overline{Y} + \overline{X} \cdot Y = X \oplus Y$$

$$S = (X + Y) \cdot (\overline{X} + \overline{Y})$$

- and


$$C = X \cdot Y$$

$$C = \overline{(\overline{(X \cdot Y)})}$$

# Implementations: Half-Adder


- The most common half adder implementation is:

$$S = X \oplus Y$$
$$C = X \cdot Y$$

 

- A NAND only implementation is:
 
$$S = (X + Y) \cdot C$$
$$C = ((X \cdot Y))$$



# Functional Block: Full-Adder

---

- A full adder is similar to a half adder, but includes a carry-in bit from lower stages. Like the half-adder, it computes a sum bit, S and a carry bit, C.

- For a carry-in (Z) of 0, it is the same as the half-adder:

Z	0	0	0	0
X	0	0	1	1
<u>+ Y</u>	<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>	<u>+ 1</u>
C S	0 0	0 1	0 1	1 0

- For a carry- in (Z) of 1:

Z	1	1	1	1
X	0	0	1	1
<u>+ Y</u>	<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>	<u>+ 1</u>
C S	0 1	1 0	1 0	1 1

# Logic Optimization: Full-Adder

## ■ Full-Adder Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## ■ Full-Adder K-Map:

		Y			
		0		1	
X	0		1		1
	1	1		1	
		Z			

		Y			
		0		1	
X	0			1	
	1	1	1	1	
		Z			

# Equations: Full-Adder

---

- From the K-Map, we get:

$$S = X \overline{Y} \overline{Z} + \overline{X} Y \overline{Z} + \overline{X} \overline{Y} Z + X Y Z$$

$$C = X Y + X Z + Y Z$$

- The S function is the three-bit XOR function (Odd Function):

$$S = X \oplus Y \oplus Z$$

- The Carry bit C is 1 if both X and Y are 1 (the sum is 2), or if the sum is 1 and a carry-in (Z) occurs. Thus C can be re-written as:

$$C = X Y + (X \oplus Y) Z$$


- The term  $X \cdot Y$  is *carry generate*.
- The term  $X \oplus Y$  is *carry propagate*.

# Implementation: Full Adder

- Full Adder Schematic
- Here  $X$ ,  $Y$ , and  $Z$ , and  $C$  (from the previous pages) are  $A$ ,  $B$ ,  $C_i$  and  $C_o$ , respectively. Also,  
     $G$  = generate and  
     $P$  = propagate.
- Note: This is really a combination of a 3-bit odd function (for  $S$ ) and Carry logic (for  $C_o$ ):

( $G$  = Generate) OR ( $P$  = Propagate AND  $C_i$  = Carry In)

$$C_o = G + P \cdot C_i$$

 




# Binary Adders

- To add multiple operands, we “bundle” logical signals together into vectors and use functional blocks that operate on the vectors
- Example: 4-bit ripple carry adder: Adds input vectors  $A(3:0)$  and  $B(3:0)$  to get a sum vector  $S(3:0)$
- Note: carry out of cell  $i$  becomes carry in of cell  $i + 1$

Description	Subscript 3 2 1 0	Name
Carry In	0 1 1 0	$C_i$
Augend	1 0 1 1	$A_i$
Addend	<u>0 0 1 1</u>	$B_i$
Sum	1 1 1 0	$S_i$
Carry out	0 0 1 1	$C_{i+1}$

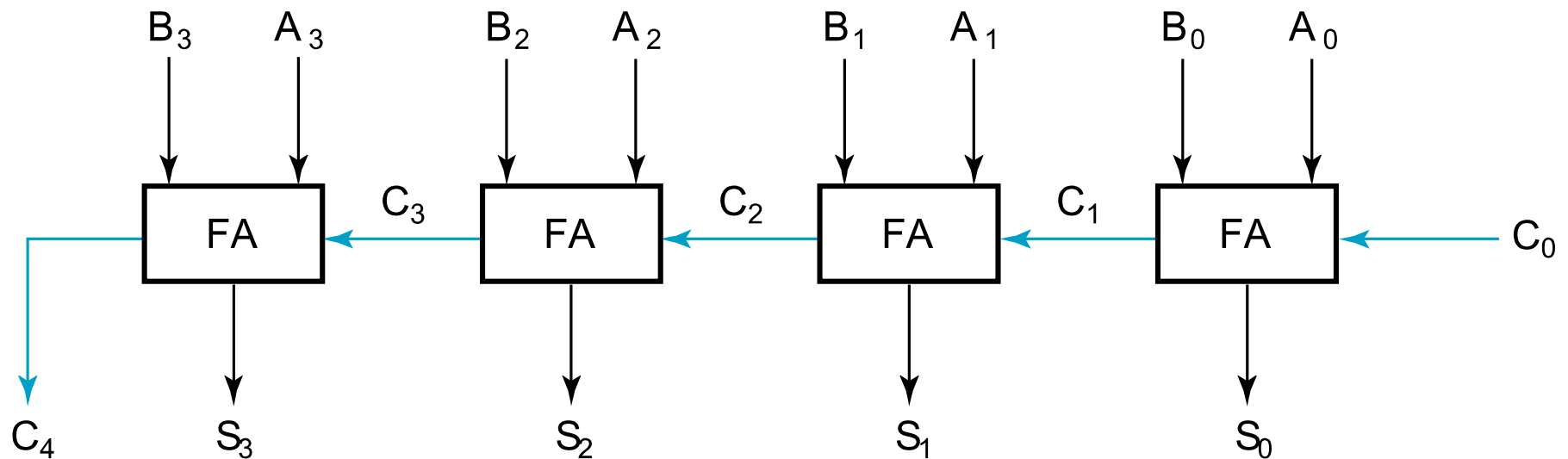
# 4-bit Ripple-Carry Binary Adder

- A four-bit Ripple Carry Adder made from four 1-bit Full Adders:


 
# Carry Propagation & Delay


- One problem with the addition of binary numbers is the length of time to propagate the ripple carry from the least significant bit to the most significant bit.
- The gate-level propagation path for a 4-bit ripple carry adder of the last example:



- Note: The "long path" is from  $A_0$  or  $B_0$  through the circuit to  $S_3$ .
 
# Carry Lookahead

- Given Stage  $i$  from a Full Adder, we know that there will be a carry generated when  $A_i = B_i = "1"$ , whether or not there is a carry-in.
- Alternately, there will be a carry propagated if the “half-sum” is “1” and a carry-in,  $C_i$  occurs.
- These two signal conditions are called *generate*, denoted as  $G_i$ , and *propagate*, denoted as  $P_i$  respectively and are identified in the circuit:



# Carry Lookahead (continued)

---

- In the ripple carry adder:
  - $G_i$ ,  $P_i$ , and  $S_i$  are local to each cell of the adder
  - $C_i$  is also local each cell
- In the carry lookahead adder, in order to reduce the length of the carry chain,  $C_i$  is changed to a more global function spanning multiple cells
- Defining the equations for the Full Adder in term of the  $P_i$  and  $G_i$ :

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

# Carry Lookahead Development

---

- $C_{i+1}$  can be removed from the cells and used to derive a set of carry equations spanning multiple cells.
- Beginning at the cell 0 with carry in  $C_0$ :

$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 = G_2 + P_2(G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 \\ &\quad + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

# Group Carry Lookahead Logic

---

- Figure 5-6 in the text shows the implementation of these equations for four bits. This could be extended to more than four bits; in practice, due to limited gate fan-in, such extension is not feasible.
- Instead, the concept is extended another level by considering *group generate* ( $G_{0-3}$ ) and *group propagate* ( $P_{0-3}$ ) functions:

$$G_{0-3} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 P_0 G_0$$

$$P_{0-3} = P_3 P_2 P_1 P_0$$

- Using these two equations:

$$C_4 = G_{0-3} + P_{0-3} C_0$$

- Thus, it is possible to have four 4-bit adders use one of the same carry lookahead circuit to speed up 16-bit addition


# Carry Lookahead Example

## ■ Specifications:

- 16-bit CLA

- Delays:

 - NOT = 1
- XOR = Isolated AND = 3
- AND-OR = 2



## ■ Longest Delays:

- Ripple carry adder\* =  $3 + 15 \times 2 + 3 = 36$
- CLA =  $3 + 3 \times 2 + 3 = 12$

\*See slide 16



# Unsigned Subtraction

---

## ■ Algorithm:


- Subtract the subtrahend  $N$  from the minuend  $M$
- If no end borrow occurs, then  $M \geq N$ , and the result is a non-negative number and correct.
- If an end borrow occurs, the  $N > M$  and the difference  $M - N + 2n$  is subtracted from  $2n$ , and a minus sign is appended to the result.

## ■ Examples:

0	1
1001	0100
– <u>0111</u>	– <u>0111</u>
0010	1101
	10000
	– <u>1101</u>
	(–) 0011
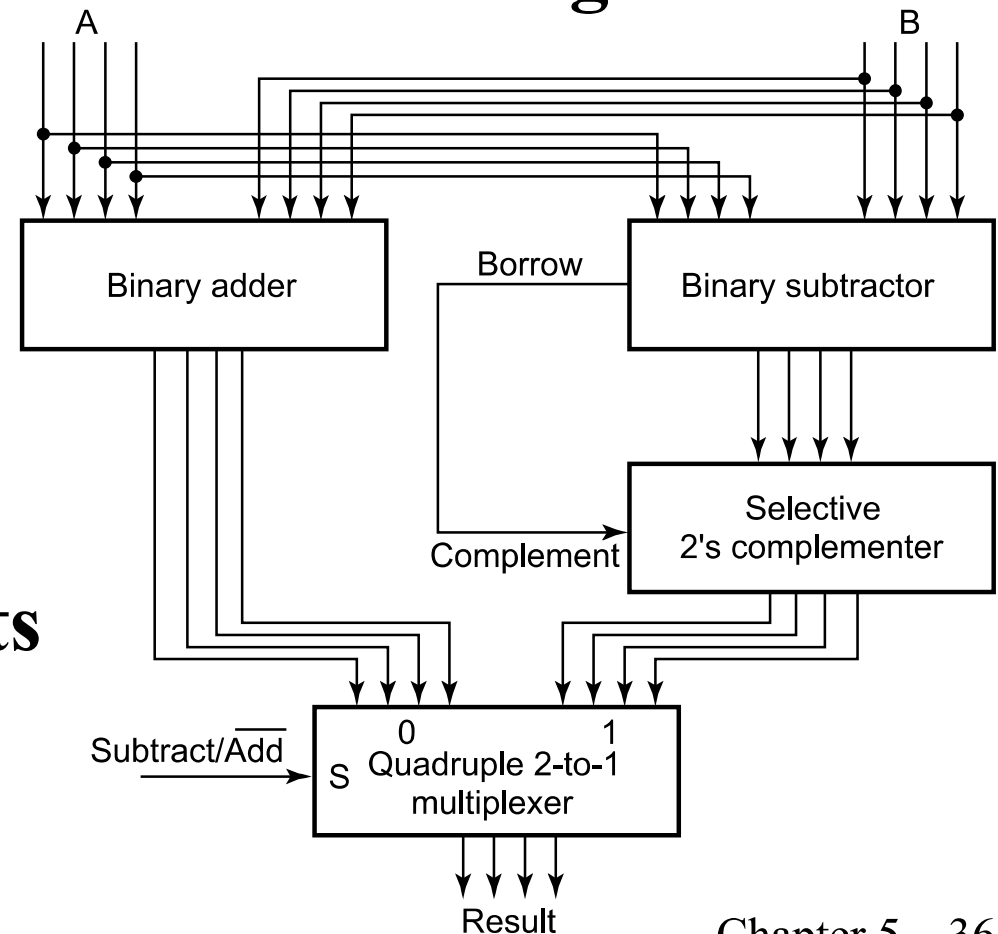
# Unsigned Subtraction (continued)

- The subtraction,  $2^n - N$ , is taking the 2's complement of N
- To do both unsigned addition and unsigned subtraction requires:
- Quite complex!
- Goal: Shared simpler logic for both addition and subtraction
- Introduce complements as an approach



# Binary 2's Complement

---

- For  $r = 2$ ,  $N = 01110011_2$ ,  $n = 8$  (8 digits), we have:

$$(r^n) = 256_{10} \text{ or } 100000000_2$$

- The 2's complement of 01110011 is then:

$$\begin{array}{r} 100000000 \\ - 01110011 \\ \hline 10001101 \end{array}$$

- Note the result is the 1's complement plus 1, a fact that can be used in designing hardware

# Subtraction with 2's Complement

---

- For n-digit, unsigned numbers M and N, find  $M - N$  in base 2:
  - Add the 2's complement of the subtrahend N to the minuend M:
$$M + (2^n - N) = M - N + 2^n$$
  - If  $M \geq N$ , the sum produces end carry  $r^n$  which is discarded; from above,  $M - N$  remains.
  - If  $M < N$ , the sum does not produce an end carry and, from above, is equal to  $2^n - (N - M)$ , the 2's complement of  $(N - M)$ .
  - To obtain the result  $-(N - M)$ , take the 2's complement of the sum and place a  $-$  to its left.

# Unsigned 2's Complement Subtraction Example 1

---


- Find  $01010100_2 - 01000011_2$

$$\begin{array}{r} 01010100 \\ - 01000011 \\ \hline \end{array} \xrightarrow{\text{2's comp}} \begin{array}{r} 1\ 01010100 \\ + 10111101 \\ \hline 00010001 \end{array}$$

- The carry of 1 indicates that no correction of the result is required.
 
# 2's Complement Adder/Subtractor

- Subtraction can be done by addition of the 2's Complement.
  1. Complement each bit (1's Complement.)
  2. Add 1 to the result.
- The circuit shown computes  $A + B$  and  $A - B$ :
- For  $S = 1$ , subtract, the 2's complement of  $B$  is formed by using XORs to form the 1's comp and adding the 1 applied to  $C_0$ .
- For  $S = 0$ , add,  $B$  is passed through unchanged



# Overflow Detection

---

- ***Overflow* occurs if  $n + 1$  bits are required to contain the result from an  $n$ -bit addition or subtraction**
- **Overflow can occur for:**
  - Addition of two operands with the same sign
  - Subtraction of operands with different signs
- **Signed number overflow cases with correct result sign**

0	0	1	1
+ <u>0</u>	- <u>1</u>	- <u>0</u>	+ <u>1</u>
0	0	1	1
- **Detection can be performed by examining the result signs which should match the signs of the top operand**

# Overflow Detection

- Signed number cases with carries  $C_n$  and  $C_{n-1}$  shown for correct result signs:

$$\begin{array}{r}
 0 \ 0 \ 0 \ 0 \ 1 \ 1 \ 1 \\
 0 \quad 0 \quad 1 \quad 1 \\
 + \underline{0} \quad - \underline{1} \quad - \underline{0} \quad + \underline{1} \\
 0 \quad 0 \quad 1 \quad 1
 \end{array}$$

- Signed number cases with carries shown for erroneous result signs (indicating overflow):

$$\begin{array}{r}
 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \\
 0 \quad 0 \quad 1 \quad 1 \\
 + \underline{0} \quad - \underline{1} \quad - \underline{0} \quad + \underline{1} \\
 1 \quad 1 \quad 0 \quad 0
 \end{array}$$

- Simplest way to implement overflow  $V = C_n \oplus C_{n-1}$
- This works correctly only if 1's complement and the addition of the carry in of 1 is used to implement the complementation! Otherwise fails for  $-10 \dots 0$



# Binary Multiplication

---

- The binary digit multiplication table is trivial:

$(a \times b)$	$b = 0$	$b = 1$
$a = 0$	0	0
$a = 1$	0	1

- This is simply the Boolean AND function.
- Form larger products the same way we form larger products in base 10.

## Review - Decimal Example: $(237 \times 149)_{10}$

- **Partial products are:**  $237 \times 9$ ,  $237 \times 4$ ,  
and  $237 \times 1$

- **Note that the partial product summation for  $n$  digit, base 10 numbers requires adding up to  $n$  digits (with carries).**

- **Note also  $n \times m$  digit multiply generates up to an  $m + n$  digit result.**

			<b>2</b>	<b>3</b>	<b>7</b>
<b>Product</b>	<b>×</b>	<b>1</b>	<b>4</b>	<b>9</b>	
<b>base 10</b>		<b>2</b>	<b>1</b>	<b>3</b>	<b>3</b>
<b>g up</b>		<b>9</b>	<b>4</b>	<b>8</b>	<b>-</b>
<b>• +</b>	<b>2</b>	<b>3</b>	<b>7</b>	<b>-</b>	<b>-</b>
		<b>3</b>	<b>5</b>	<b>3</b>	<b>1</b>
					<b>3</b>

# Binary Multiplication Algorithm

---

- **We execute radix 2 multiplication by:**
  - Computing partial products, and
  - Justifying and summing the partial products. (same as decimal)
- **To compute partial products:**
  - Multiply the row of multiplicand digits by each multiplier digit, one at a time.
  - With binary numbers, partial products are very simple! They are either:
    - all zero (if the multiplier digit is zero), or
    - the same as the multiplicand (if the multiplier digit is one).
- **Note: No carries are added in partial product formation!**

# Example: (101 x 011) Base 2

- Partial products are:  $101 \times 1$ ,  $101 \times 1$ , and  $101 \times 0$

- Note that the partial product summation for  $n$  digit, base 2 numbers requires adding up to  $n$  digits (with carries) in a column.

$$\begin{array}{r}
 \phantom{\times} \phantom{00} 1 \phantom{00} 0 \phantom{00} 1 \\
 \times \phantom{00} 0 \phantom{00} 1 \phantom{00} 1 \\
 \hline
 \phantom{\times} \phantom{00} 1 \phantom{00} 0 \phantom{00} 1 \\
 \phantom{\times} 1 \phantom{00} 0 \phantom{00} 1 \\
 \phantom{\times} 0 \phantom{00} 0 \phantom{00} 0 \\
 \hline
 \phantom{\times} 0 \phantom{00} 0 \phantom{00} 1 \phantom{00} 1 \phantom{00} 1 \phantom{00} 1
 \end{array}$$

- Note also  $n \times m$  digit multiply generates up to an  $m + n$  digit result (same as decimal).

# Multiplier Boolean Equations

- We can also make an  $n \times m$  “block” multiplier and use that to form partial products.
- Example:  $2 \times 2$  – The logic equations for each partial-product binary digit are shown below:
- We need to “add” the columns to get the product bits  $P_0$ ,  $P_1$ ,  $P_2$ , and  $P_3$ .
- Note that some columns may generate carries.

	$b_1$	$b_0$	
	$a_1$	$a_0$	
	$\times$	$(a_0 \cdot b_1)$	$(a_0 \cdot b_0)$
$+$	$(a_1 \cdot b_1)$	$(a_1 \cdot b_0)$	
$P_3$	$P_2$	$P_1$	$P_0$

# Multiplier Arrays Using Adders

- An implementation of the  $2 \times 2$  multiplier array is shown:

