

Boolean Function Optimization

- ✓ Minimizing the gate input (or literal) cost of a (a set of) Boolean equation(s) reduces circuit cost.
- ✓ **We choose gate input cost.**
- ✓ Boolean Algebra and graphical techniques are tools to minimize cost criteria values.
- ✓ Some important questions:
 - When do we stop trying to reduce the cost?
 - Do we know when we have a minimum cost?
- ✓ Treat optimum or near-optimum cost functions for two-level (SOP and POS) circuits first.
- ✓ Introduce a graphical technique using Karnaugh maps (K-maps, for short)

Karnaugh Maps (K-map)

- ✓ A K-map is a collection of squares
 - Each square represents a minterm
 - The collection of squares is a graphical representation of a Boolean function
 - Adjacent squares differ in the value of one variable
 - Alternative algebraic expressions for the same function are derived by recognizing patterns of squares (corresponding to cubes)
- ✓ The K-map can be viewed as
 - A reorganized version of the truth table or a particular cube representation**

Some Uses of K-Maps

✓ Provide a means for:

- Finding optimum
 - SOP and POS standard forms, and
 - two-level AND/OR and OR/AND circuit implementationsfor functions with small numbers of variables
- Visualizing concepts related to manipulating Boolean expressions
- Demonstrating concepts used by computer-aided design programs to simplify large circuits


The Boolean Space B^n


- ✓ $B = \{0, 1\}$
- ✓ $B^2 = \{0, 1\} \times \{0, 1\} = \{00, 01, 10, 11\}$


Karnaugh Maps:

B^0 




B^1 

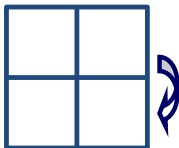B^2 

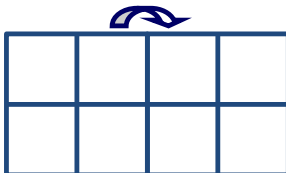B^3 

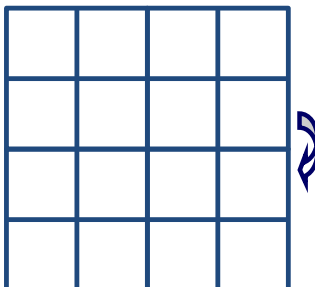B^4 

Boolean Cubes:

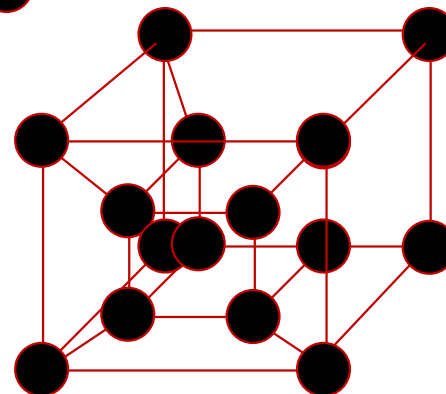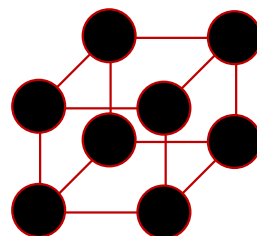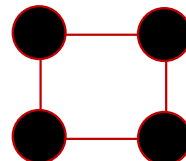

Two Variable Maps

✓ A 2-variable Karnaugh Map:

- Note that minterm m_0 and minterm m_1 are "adjacent" and differ in the value of the variable y
- Similarly, minterm m_0 and minterm m_2 differ in the x variable.
- Also, m_1 and m_3 differ in the x variable as well.
- Finally, m_2 and m_3 differ in the value of the variable y

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	m_0 $\bar{x} \bar{y}$	m_1 $\bar{x} y$
$x = 1$	m_2 $x \bar{y}$	m_3 $x y$

K-Map and Truth Tables

- ✓ The K-Map is just a different form of the truth table.
- ✓ Example - Two variable function:
 - We choose a, b, c and d from the set $\{0,1\}$ to implement a particular function, $F(x,y)$.

Function Table

Input Values (x,y)	Function Value $F(x,y)$
0 0	a
0 1	b
1 0	c
1 1	d

K-Map

$x \backslash y$	$y = 0$	$y = 1$
$x = 0$	a	b
$x = 1$	c	d

K-Map Function Representation

✓ Example: $F(x,y) = x$

$F = x$	$y = 0$	$y = 1$
$x = 0$	0	0
$x = 1$	1	1

✓ For function $F(x,y)$, the two adjacent cells containing 1's can be combined using the Minimization Theorem:

$$F(x,y) = x\bar{y} + xy = x$$

K-Map Function Representation

✓ Example: $G(x,y) = \bar{x}y + x\bar{y} + xy$

$G=x+y$	$y = 0$	$y = 1$
$x = 0$	0	1
$x = 1$	1	1


✓ For $G(x,y)$, two pairs of adjacent cells containing 1's can be combined using the Minimization Theorem:

$$G(x,y) = (x\bar{y} + xy) + (\bar{x}y + xy) = x + y$$

Duplicate xy

Three Variable Maps

- ✓ A three-variable K-map:

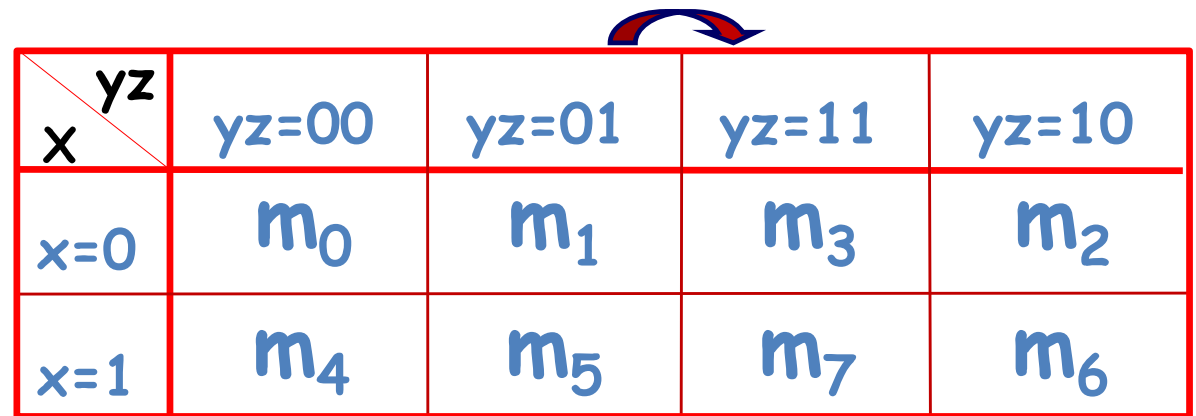

$x \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$x=0$	m_0	m_1	m_3	m_2
$x=1$	m_4	m_5	m_7	m_6

- ✓ Where each minterm corresponds to the product terms:

$x \backslash yz$	$yz=00$	$yz=01$	$yz=11$	$yz=10$
$x=0$	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
$x=1$	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

- ✓ Note that if the binary value for an index differs in one bit position, the minterms are adjacent on the K-Map

Alternative Map Labeling

- ✓ Map use largely involves:
 - Entering values into the map, and
 - Reading off product terms from the map.
- ✓ Alternate labelings are useful:


$y \ z$				
\bar{y}			y	
\bar{x}	0	1	3	2
x	4	5	7	6
	\bar{z}	z	\bar{z}	

		$y \ z$			
		00	01	11	10
x	0	0	1	3	2
	1	4	5	7	6
		z			

Example: Combining Squares

✓ Example: Let

✓ $F(x, y, z) = \sum_m (2, 3, 6, 7)$

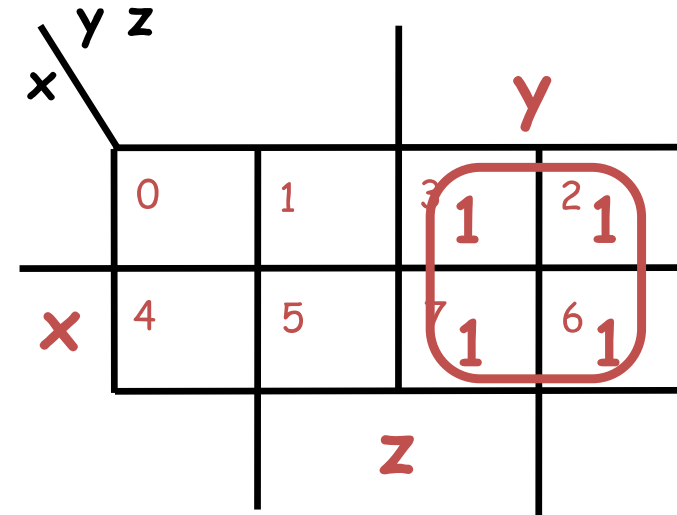

✓ Applying the Minimization Theorem three times:

$$\begin{aligned} F(x, y, z) &= \bar{x} y z + x y z + \bar{x} y \bar{z} + x y \bar{z} \\ &= yz + y\bar{z} \\ &= y \end{aligned}$$

✓ Thus the four terms that form a 2×2 square correspond to the term "y".

Combining Squares

- ✓ By combining squares, we reduce number of literals in a product term, reducing the literal cost, thereby reducing the other two cost criteria
- ✓ On a 3-variable K-Map:
 - One square represents a minterm with three variables
 - Two adjacent squares represent a cube that is product term with two variables
 - Four "adjacent" terms represent a cube that is product term with one variable
 - Eight "adjacent" terms is the function of all ones (no variables) is a tautology $f^1=1$.


Example Functions

- ✓ By convention, we represent the minterms of F by a "1" in the map and leave the minterms of blank \bar{F}

- ✓ Example:

$$F(x, y, z) = \sum_m (2, 3, 4, 5)$$

$$F(x, y, z) = \bar{x}y + x\bar{y}$$

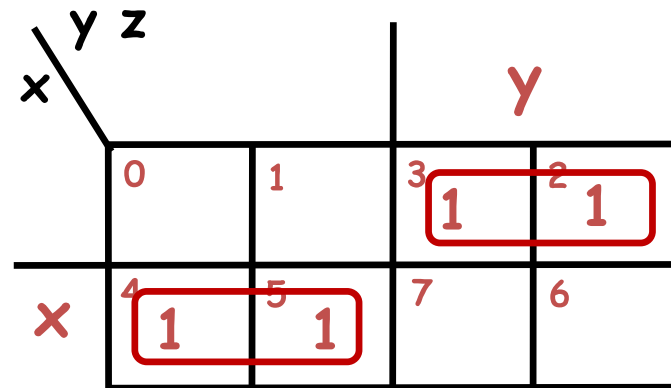


- ✓ Example:

- ✓ $F(x, y, z) = \sum_m (3, 4, 6, 7)$

- ✓ $F(x, y, z) = yz + x\bar{z}$

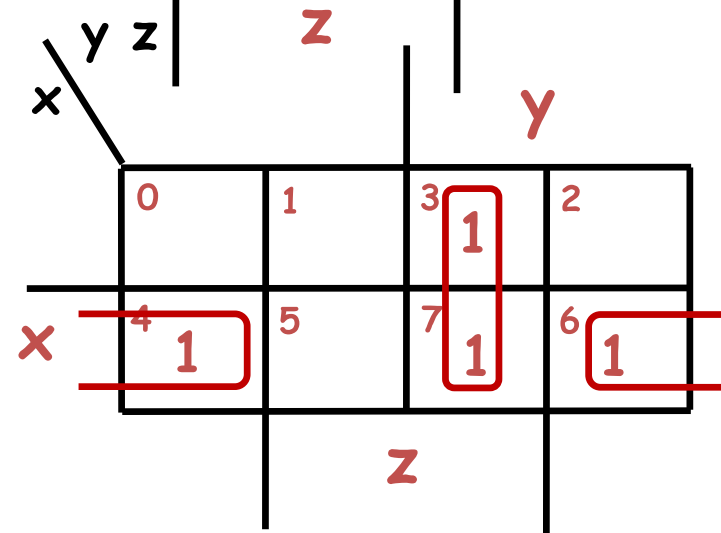- ✓ Learn the locations of the 8 indices based on the variable order shown (x, most significant and z, least significant) on the map boundaries




Three-Variable Maps

- ✓ Reduced literal product terms for SOP standard forms correspond to cubes i.e. to **rectangles** on the K-maps containing cell counts that are powers of 2.
- ✓ Rectangles of 2 cells represent 2 adjacent minterms; of 4 cells represent 4 minterms that form a "pairwise adjacent" ring.


Three-Variable Maps

- ✓ Topological warps of 3-variable K-maps that show *all* adjacencies:

- Venn Diagram

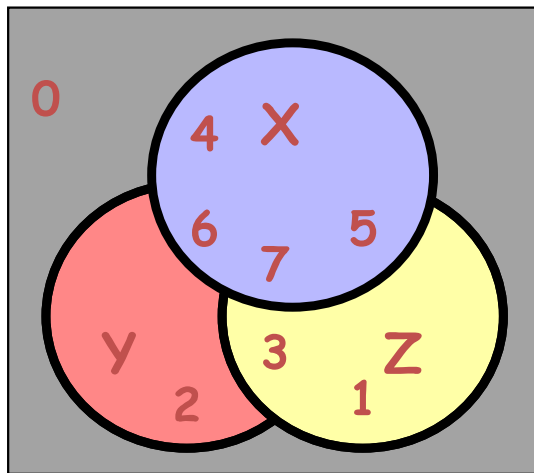


- Cylinder

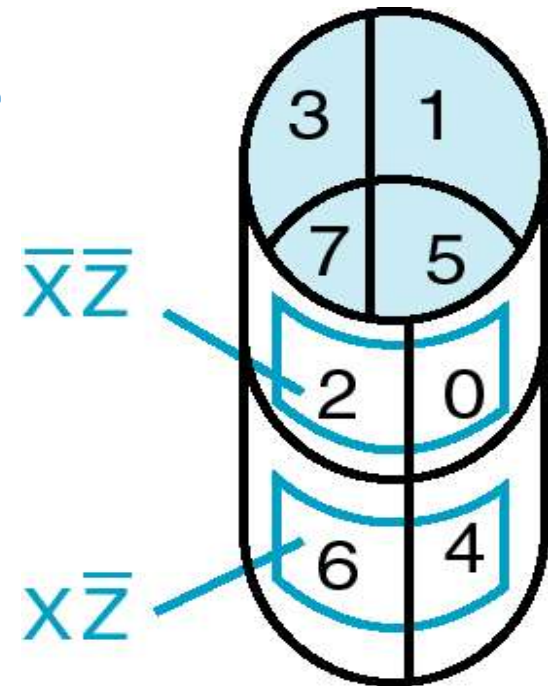

		\bar{y}		y	
x	\bar{x}	0	1	3	2
	x	4	5	7	6
		\bar{z}	z	\bar{z}	

Three-Variable Maps

- ✓ Example Shapes of 2-cell Rectangles:

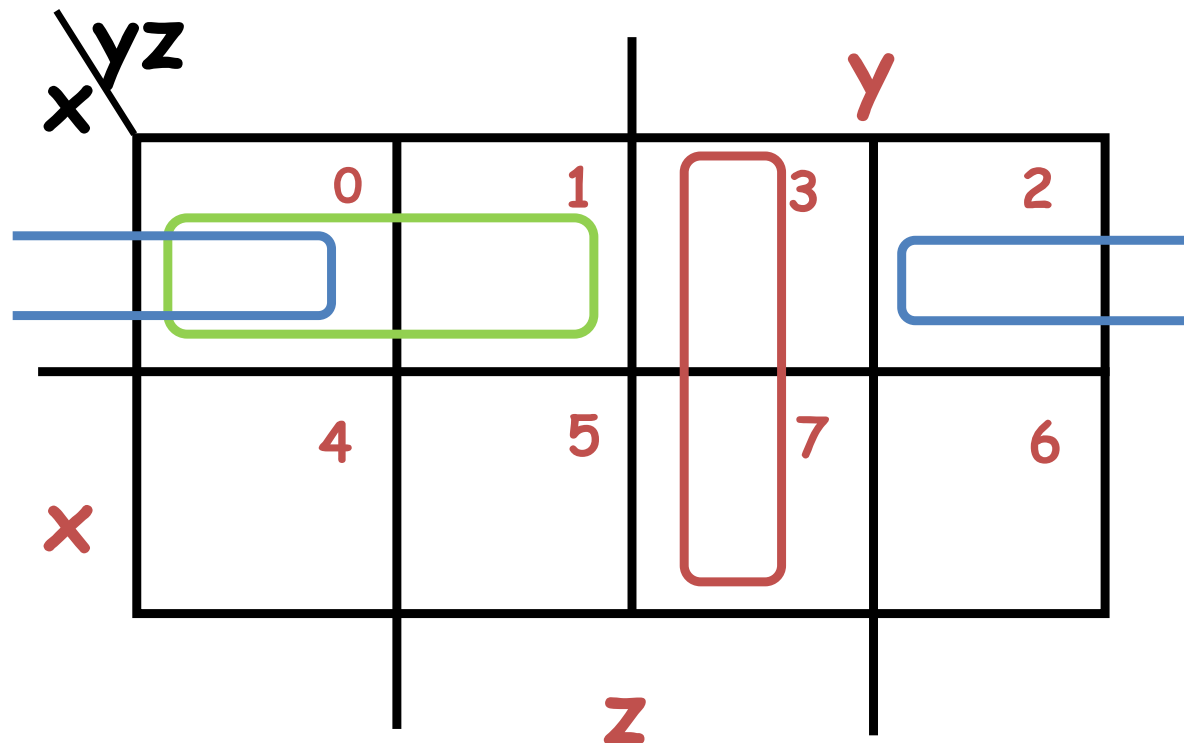


- ✓ Read off the product terms for the rectangles shown

$x'z'$ $x'y'$ yz

Three-Variable Maps

- ✓ Example Shapes of 4-cell Rectangles:

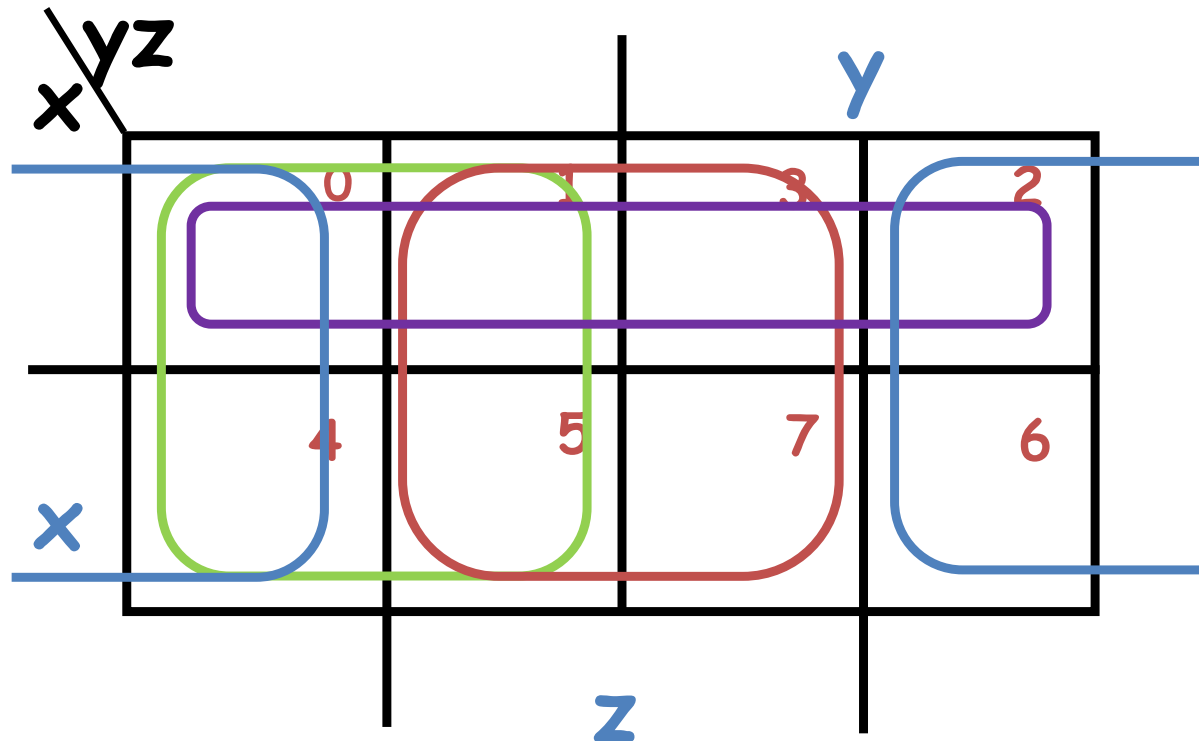


- ✓ Read off the product terms for the rectangles shown

z' z x' y'

Three Variable Maps

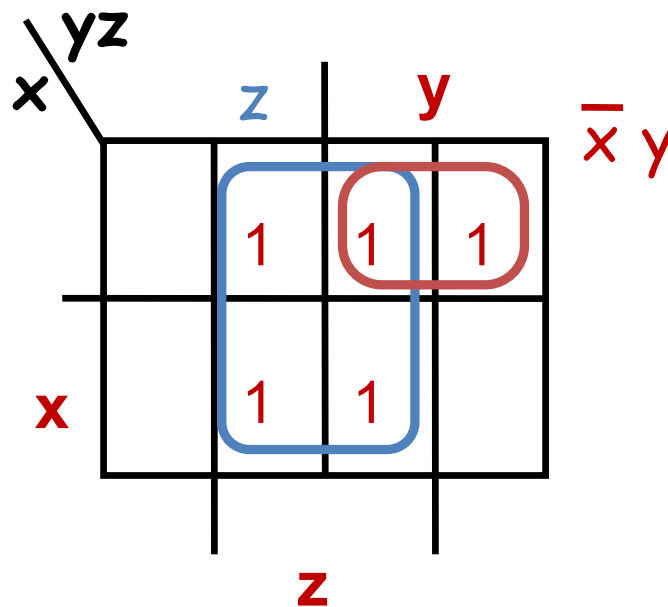- ✓ K-Maps can be used to simplify Boolean functions by a systematic methods. Terms are selected to cover the "1s" in the map.
- ✓ Example: Simplify $F(x, y, z) = \sum_m (1, 2, 3, 5, 7)$




$$F(x, y, z) = z + \bar{x}y$$

Three-Variable Map Simplification

- ✓ Use a K-map to find an optimum SOP equation for

$$F(x, y, z) = \sum_m (0, 1, 2, 4, 6, 7)$$

$$F = \bar{z} + \bar{x}\bar{y} + xy$$

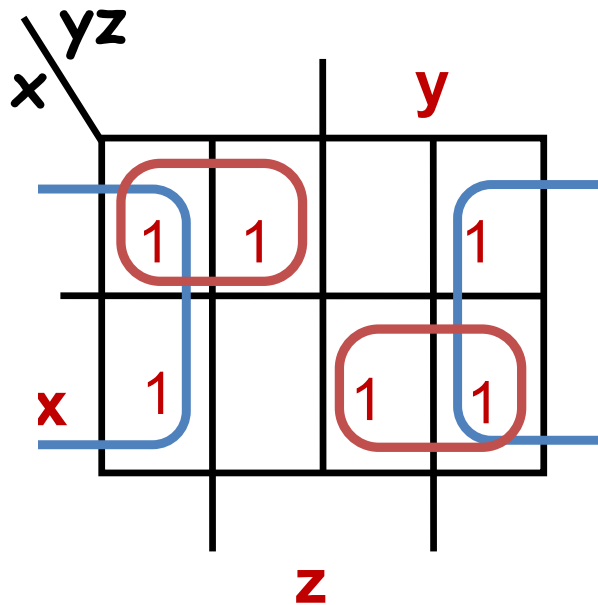

Four Variable Maps

- ✓ Map and location of minterms:

$wx \backslash yz$					
		$yz=00$	$yz=01$	$yz=11$	$yz=10$
$wx=00$		0	1	3	2
$wx=01$		4	5	7	6
$wx=11$		12	13	15	14
$wx=10$		8	9	11	10


Diagram illustrating the location of minterms in a 4-variable Karnaugh map. The map is a 4x4 grid with rows labeled wx and columns labeled yz . The minterms are numbered 0 through 15. The map is divided into four quadrants by a vertical line. The top-left quadrant is labeled w and the bottom-right quadrant is labeled x . The top-right quadrant is labeled y and the bottom-left quadrant is labeled z . A blue 'X' mark is placed on the right side of the map, indicating a specific minterm location.

Four Variable Terms

- ✓ Four variable maps can have rectangles corresponding to:
 - A single 1 = 4 variables, (i.e. Minterm)
 - Two 1s = 3 variables,
 - Four 1s = 2 variables
 - Eight 1s = 1 variable,
 - Sixteen 1s = zero variables (i.e. Constant "1")


Four-Variable Maps

- ✓ Example Shapes of Rectangles:

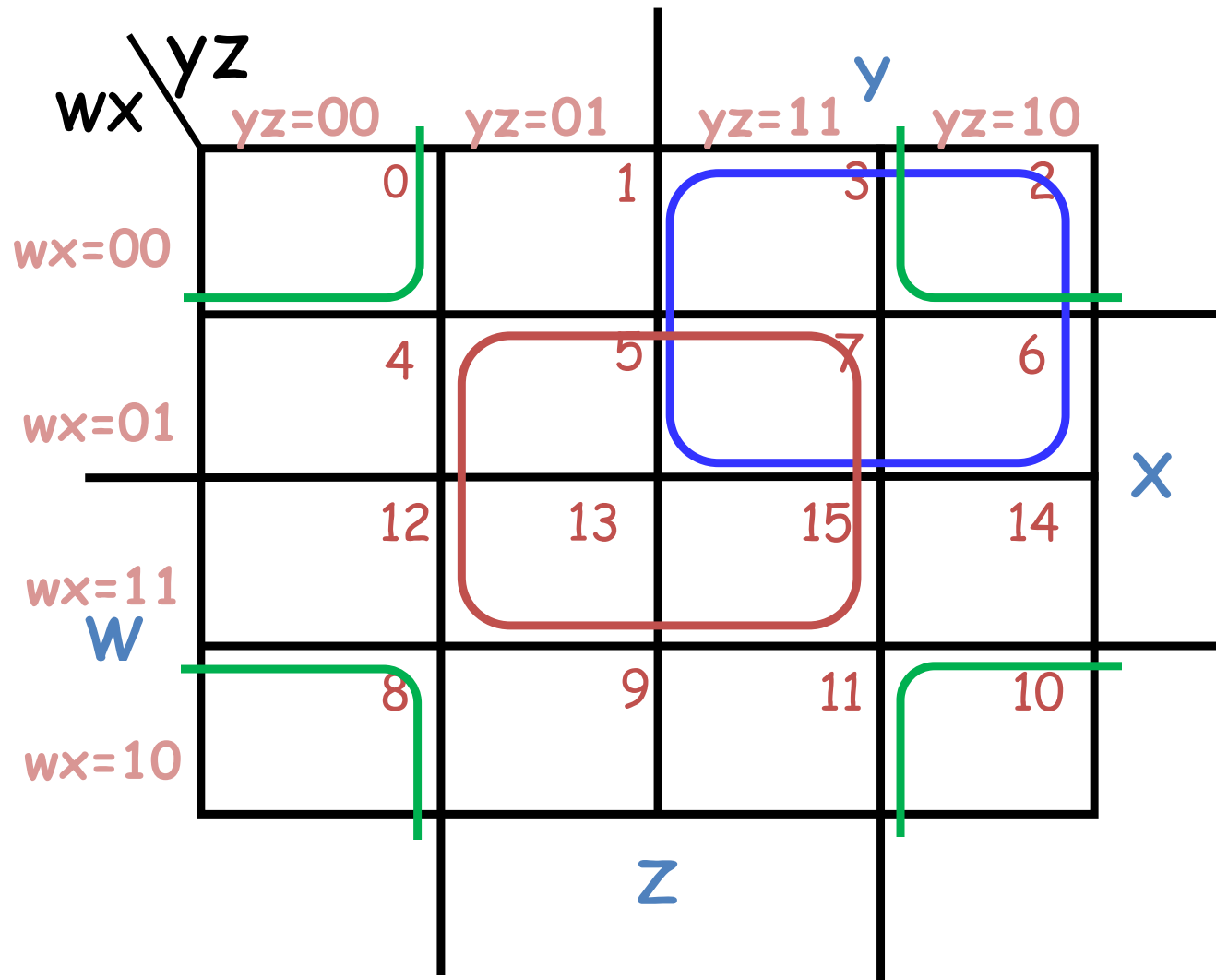


Four-Variable Maps

- ✓ Example Shapes of Rectangles:

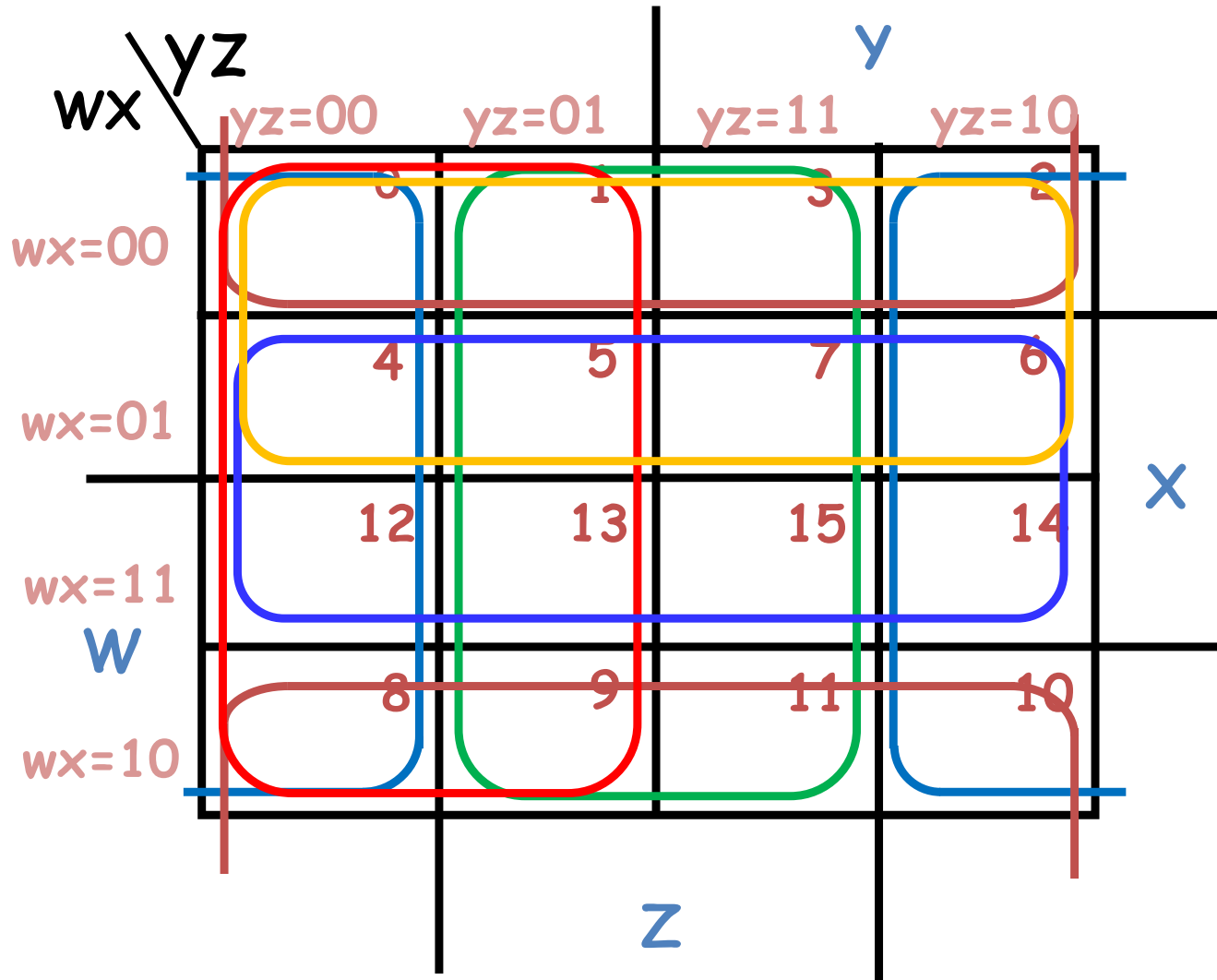


Four-Variable Map Simplification

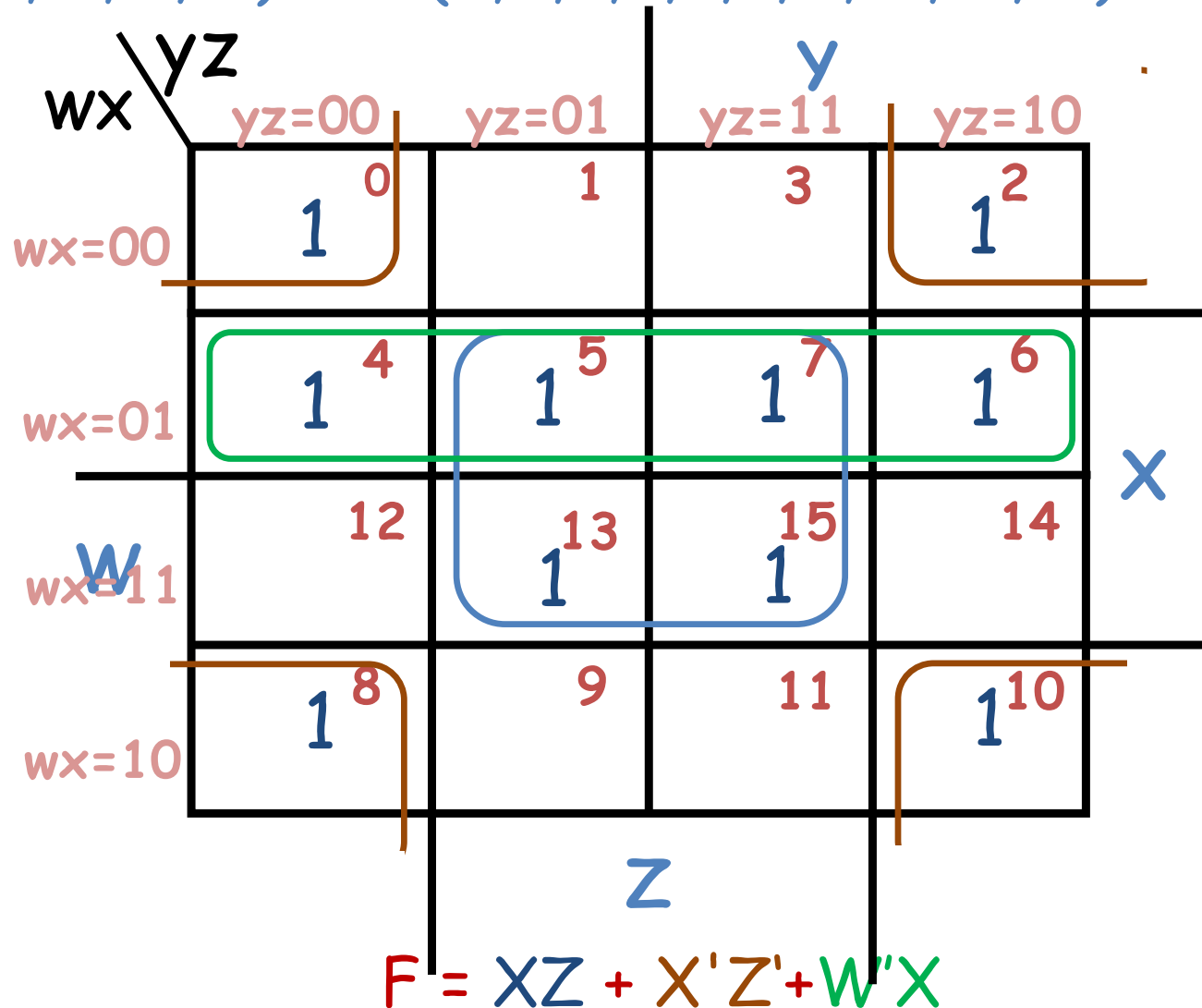✓ $F(W, X, Y, Z) = \sum_m (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$



Four-Variable Map Simplification
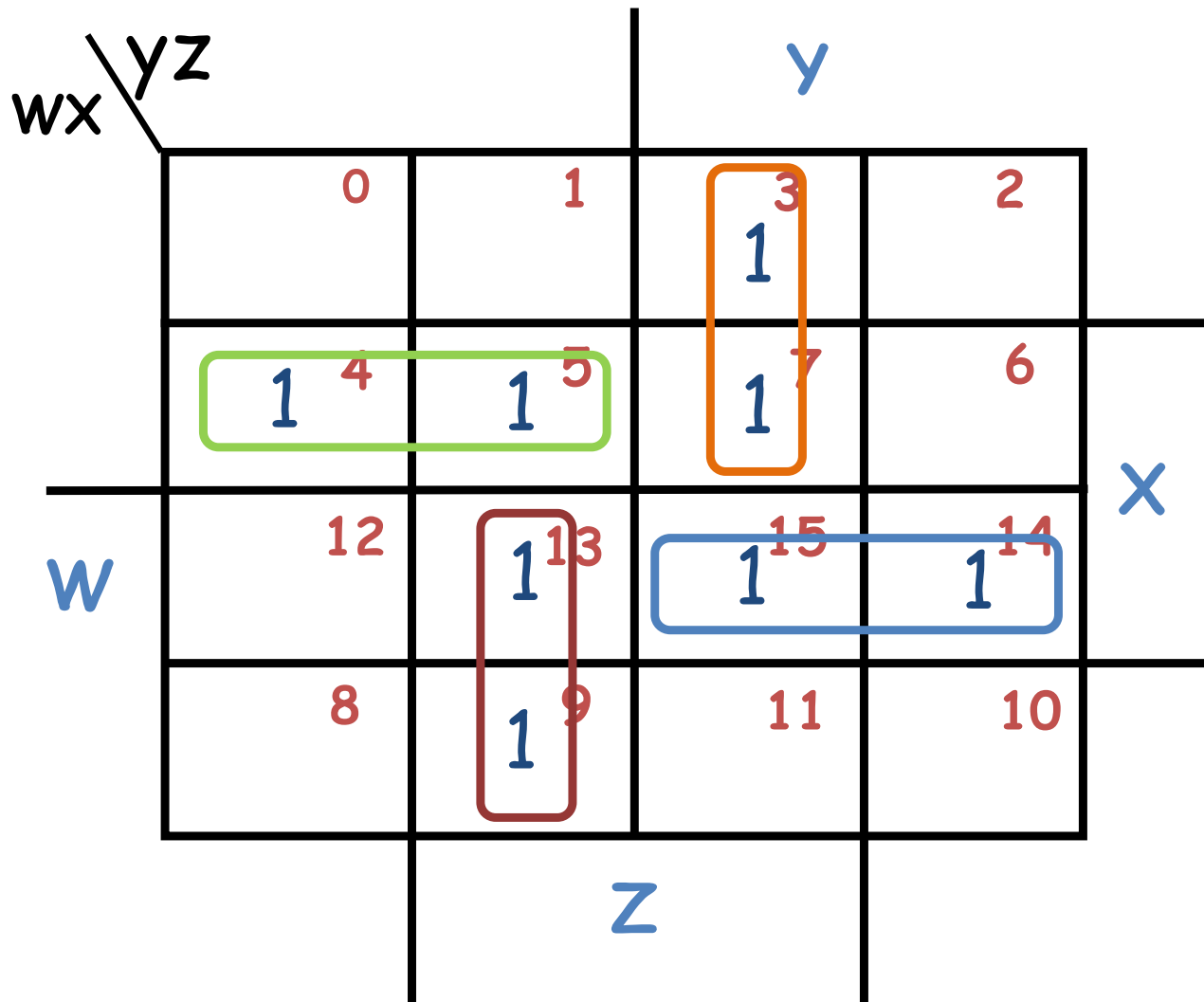
$$F(W,X,Y,Z) = \sum_m(3,4,5,7,9,13,14,15)$$




$$F = w'x'y + w'yz + wxy + wy'z$$

Systematic Simplification

- ✓ A Prime Implicant is a cube i.e. a product term obtained by combining the maximum possible number of adjacent squares in the map into a rectangle with the number of squares a power of 2.
- ✓ A prime implicant is called an Essential Prime Implicant if it is the only prime implicant that covers (includes) one or more minterms.
- ✓ Prime Implicants and Essential Prime Implicants can be determined by inspection of a K-Map.
- ✓ A set of prime implicants "*covers all minterms*" if, for each minterm of the function, at least one prime implicant in the set of prime implicants includes the minterm.


Example of Prime

✓ Find ALL Prime Implicants

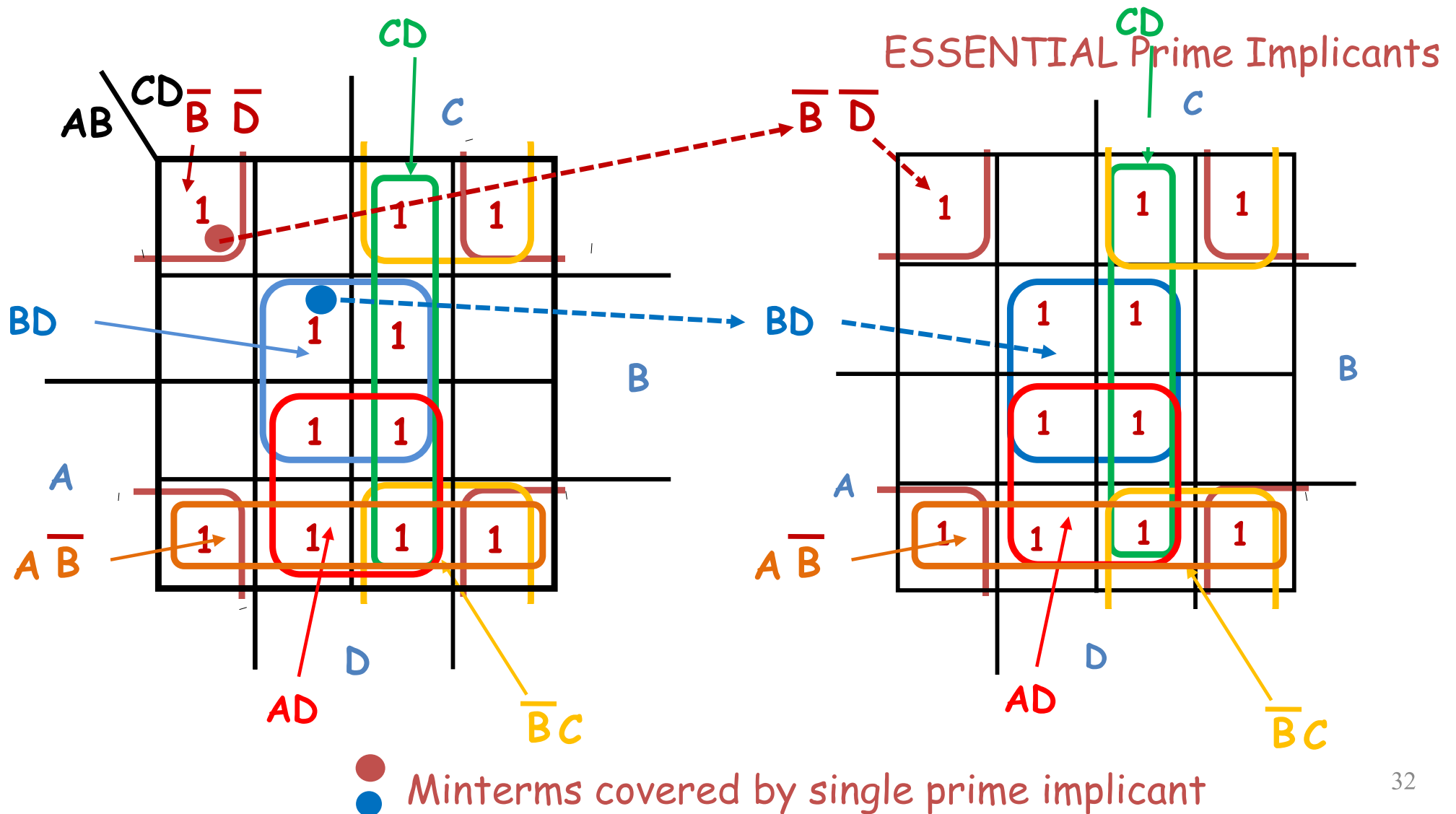

Prime Implicant Practice

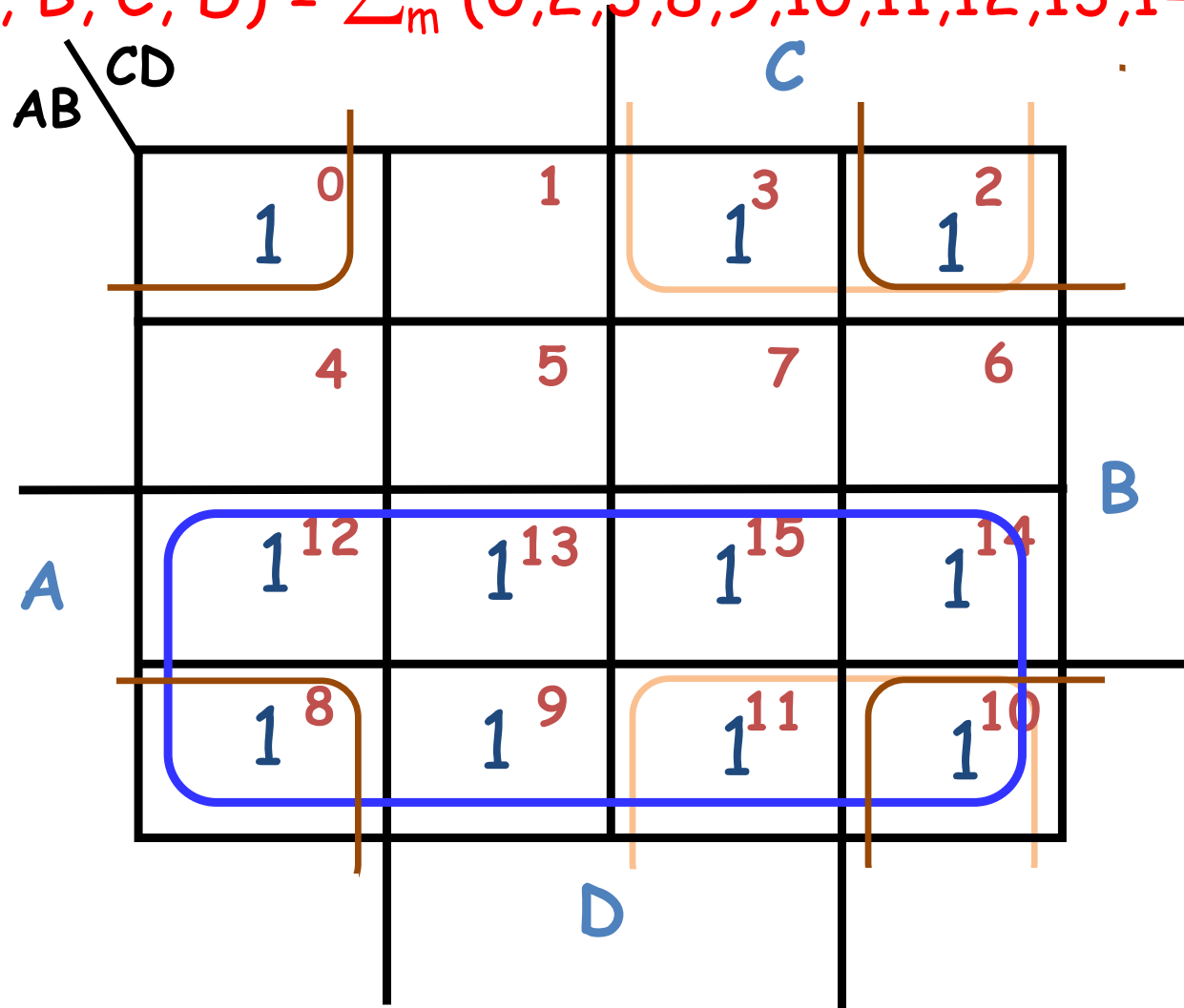- ✓ Find all prime implicants for:
- ✓ $F(A, B, C, D) = \sum_m (0, 2, 3, 8, 9, 10, 11, 12, 13, 14, 15)$




Prime implicants are: A , $\bar{B}C$, and $\bar{B}D$

Another Example

✓ Find all prime implicants for:
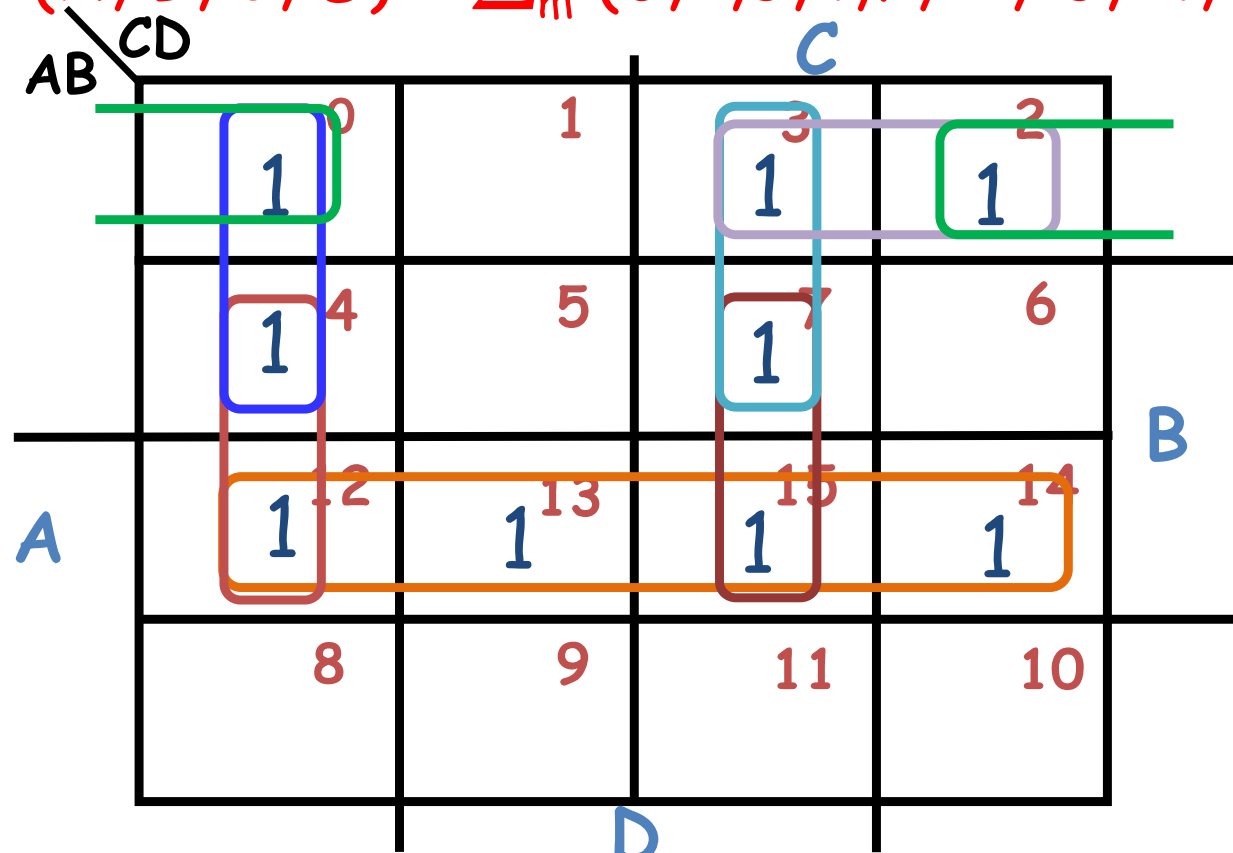
$$F(A, B, C, D) = \sum_m (0, 2, 3, 4, 7, 12, 13, 14, 15)$$



$$AB, B\overline{C}\overline{D}, \overline{A}\overline{C}\overline{D}, \overline{A}B\overline{D}, \overline{A}\overline{B}C, \overline{A}C\overline{D}, BCD$$

$$\sum_m = AB + \overline{A}\overline{C}\overline{D} + \overline{A}C\overline{D} + \overline{A}\overline{B}C \quad \sum_c = \sum_m + \overline{A}B\overline{D} + BCD + B\overline{C}\overline{D}$$